

Design of vending machine controller

Last updated: 2026-04-28 14:09:28

[L^AT_EX source here](#)

1 Design:


We have following inputs:

- X_1 : ₹5 inserted
- X_2 : ₹10 inserted

Here we assume input turns 1 when coin is being inserted and 0 when coin has been finished inserting.

The state in the system holds current "internal balance" and output. Following are internal balance values:

- 0
- 5
- 10
- ≥ 15

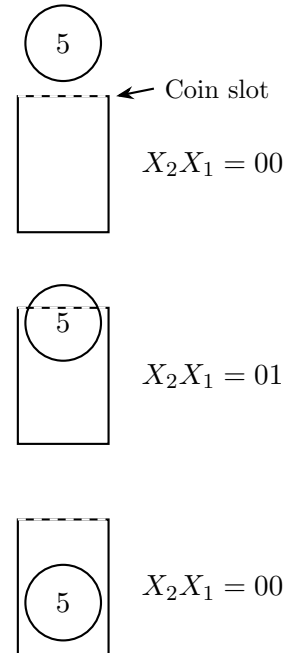


Coin insertion sequence and corresponding input.

≥ 15 value accounts for balance of 15 and 20.

2 How state transition occur

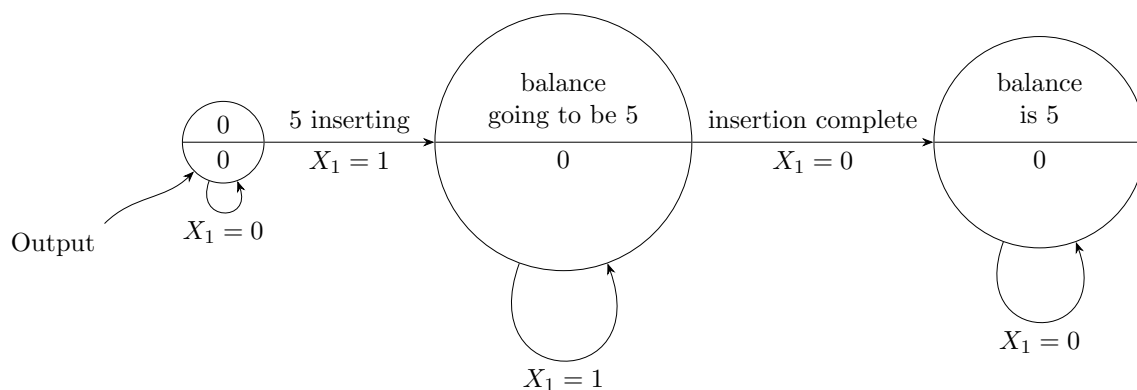
A coin insertion triggers state transition as following: (from initial state)




When coin is being inserted the system goes to a intermediate but stable state (state in the middle shown in figure). There after when coin is finished inserting it goes to another stable state where internal balance has been incremented (state in rightmost place)

Why not directly increment internal balance when coin is being inserted instead of going to a intermediate state?

You might be tempted to implement this:

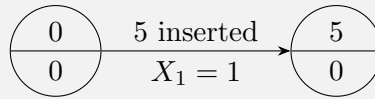

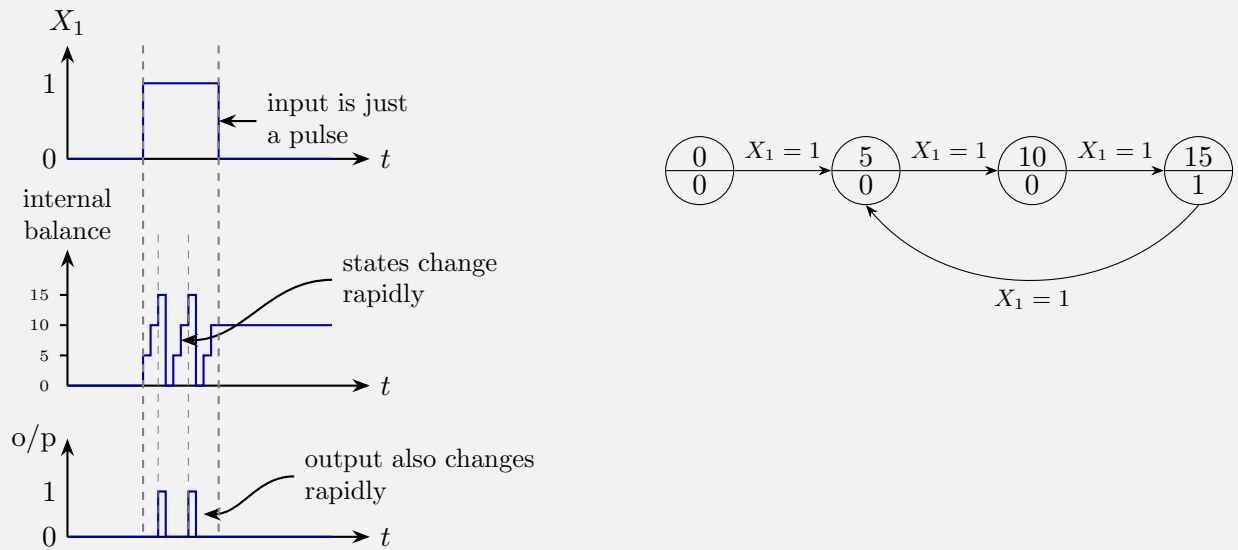It looks like it will work. But in practice this leads to a problem: how long should input be held 1? If input is held 1 for too long, the system will quickly traverse through many states in a loop even if input is just a pulse. The below figure shows what happens if $X_1 = 1$ for a brief period:



The internal state quickly switches as fast the circuit allows, hence all states become unstable when input becomes 1.

3 State Diagram & Flow table

We define states as following:


- A : initial state, balance = 0 (output = 0)
- B : balance is going to be 5 (output = 0)
- C : balance is 5 (output = 0)
- D : balance is going to be 10 (output = 0)
- E : balance is 10 (output = 0)
- F : balance is going to be ≥ 15 (output = 0)
- G : balance is ≥ 15 (output = 1)

When state G has reached, the vending machine dispenses. From G the state transition scheme is as following: if input is 5, it goes to B and if input is 10 it goes to C .

But in question it is told that the state to be reset to initial state after dispensing?

Indeed in question it is told that the state to be reset to 0. But since we are implementing a Moore machine, we cant do that directly. Because again the problem rises: what input should drive system to go from G to A while keeping the output stable for a while? This can be done only with Mealy machine where output depends on input and present state. However as you can guess, K-map simplification and circuit implementation will become very complex for output variable. Hence that requirement is carefully ignored. (This doesnt affect the overall functionality of vending machine).

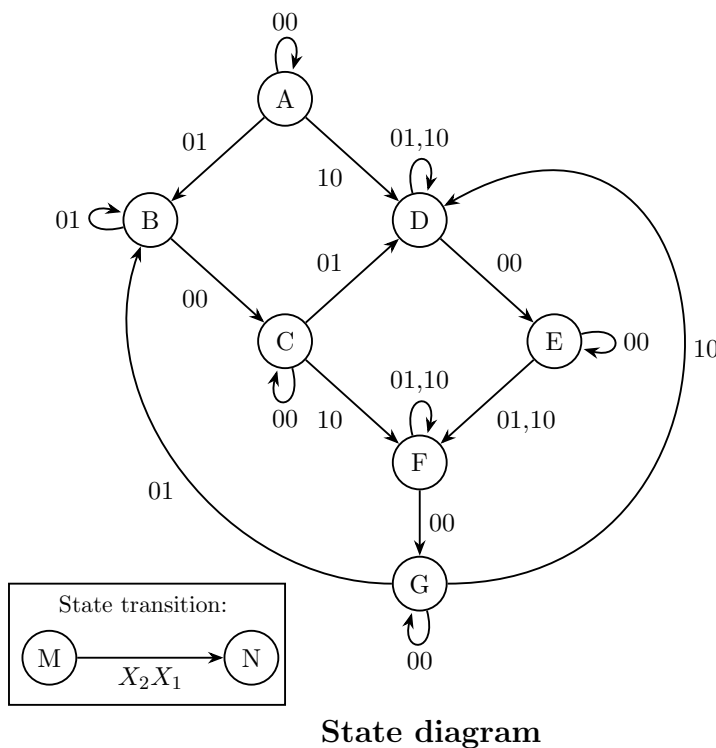Based on this we can arrive at following state diagram and Flow table.



Present State	Input X_2X_1			
	00	01	10	11
A	A, 0	B, -	D, -	-, -
B	C, -	B, 0	-, -	-, -
C	C, 0	D, -	F, -	-, -
D	E, -	D, 0	D, 0	-, -
E	E, 0	F, -	F, -	-, -
F	G, -	F, 0	F, 0	-, -
G	G, 1	B, -	D, -	-, -

Flow table

Explanation:

1. Initially system is at state A .
2. When a ₹5 is inserted the state becomes to B (as it indicates "balance is going to be ₹5") and if ₹10 was inserted the state goes to D (indicating "balance is going to be ₹10").
3. After coin has been finished inserting ($X_2X_1 = 00$) the system can go from B to C (that is "balance is 5" state). And it can only go to C as at that time only ₹5 is being inserted and no other coin can be inserted simultaneously (hence transition $X_2X_1 = 10$ is not drawn from B and is considered don't care in flow table.)
4. From C , system goes to D if ₹5 is inserted (as D indicates "balance is going to be 10") and if ₹10 is inserted it goes to F (balance is going to be $\geq$ ₹15).
5. From D , system goes to E (balance is ₹10) when either of the coin has finished inserting ($X_2X_1 = 00$).

6. From E system goes F if any of the coin is being inserted.
7. From F system goes to G (balance $is \geq ₹15$) and output $z = 1$. This is the only state where output becomes 1.
8. From G system goes to B if ₹5 is being inserted and it goes to D if ₹10 is being inserted.

State reduction is not done here, as each state already have a definite meaning, reducing it implies losing the functionality.


If you try creating implication table you'll get this

B	× AC					
C	× BD, DF	× BD				
D	× AE, BD	× CE	× CE, DF			
E	× BF, DF	× CE, BF	×, DF	× DF		
F	× AG, BF, DF	× CG	×, CG, DF	× EG	× EG	
G	×	× CG	×	× EG, BD	×	× BF, DF
	A	B	C	D	E	F

All states are incompatible with each other


4 Race free state assignment

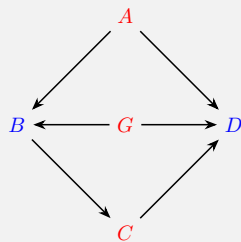If we assign binary state to 7 existing state, it will always result in a race




This is because for a grey code state assignment (ie that which produces the single bit transition between states), the states must be connected in such a way that they could be placed in the vertices of hypercube. **The maximum number of common neighbors for any pair of vertices in a hypercube is 2.** Here, states B and D are connected to **3** states (A , C , and G), hence states cannot be laid out along a hypercube of any dimension, making such 1-bit change binary state assignment impossible.

State	$S_2S_1S_0$
A	000
B	001
C	101
D	100
E	110
F	111
G	011

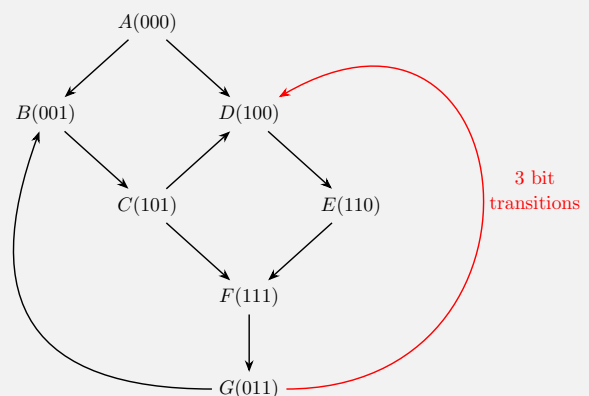

As you can see $G \rightarrow D$ transition results in multiple bit change. Hence additional state has to be added or existing states has to be split.

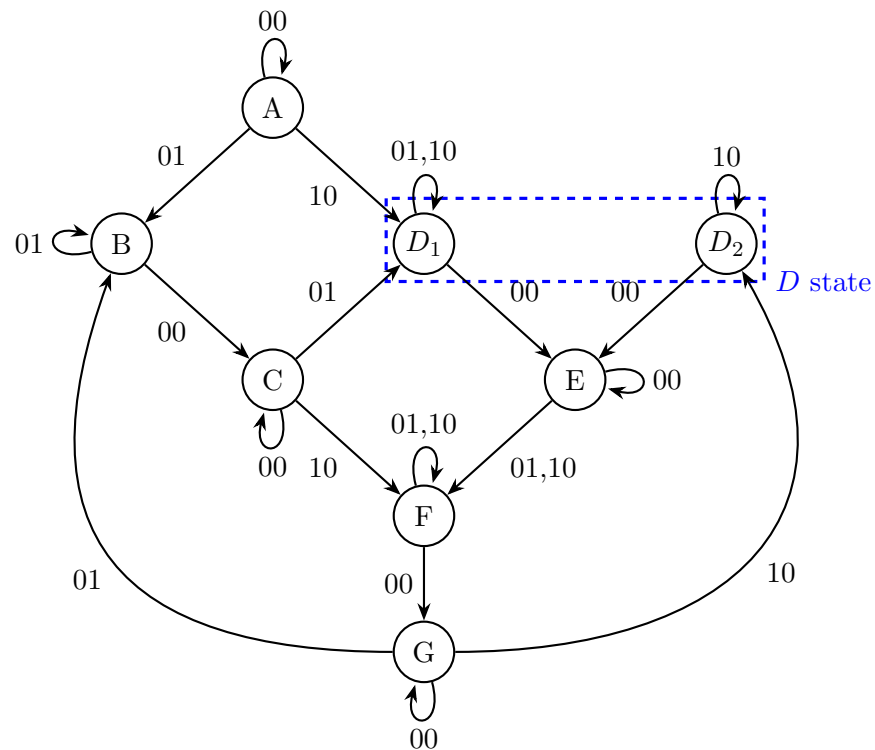To obtain race free assignment, state D is split to D_1 and D_2 in following manner:




The meaning of the states are not changed that much. D_1 and D_2 now still refers to "balance is going to be 10". But in case of D_2 the state doesn't have to handle input sequence $X_2X_1 = 01$ (₹5 is being inserted) as ₹5 can never be simultaneously inserted while ₹10 is being inserted. Hence we obtain following **modified flow table**

Present State	Input X_2X_1			
	00	01	10	11
A	A, 0	B, -	D_1 , -	-,-
B	C, -	B, 0	-,-	-,-
C	C, 0	D_1 , -	F, -	-,-
D_1	E, -	D_1 , 0	D_1 , 0	-,-
D_2	E, -	-,-	D_2 , 0	-,-
E	E, 0	F, -	F, -	-,-
F	G, -	F, 0	F, 0	-,-
G	G, 1	B, -	D_2 , -	-,-

From this following binary assignment is race free:

State	$S_2S_1S_0$
A	000
B	001
C	011
D_1	010
D_2	100
E	110
F	111
G	101

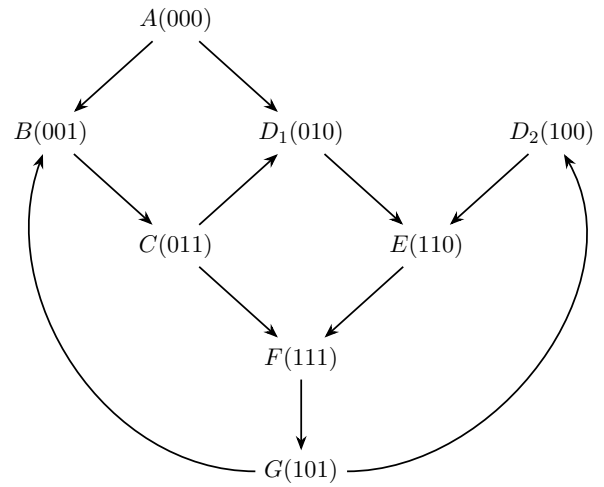

5 State transition table

The entries are rearranged to make picking the values for k-map easier

$S_2S_1S_0$	Input X_2X_1			
	00	01	11	10
000	000	001	---	010
001	011	001	---	---
011	011	010	---	111
010	110	010	---	010
100	110	---	---	100
101	101	001	---	100
111	101	111	---	111
110	110	111	---	111

6 K-Maps for Next State variables

K-map for S'_2 :

S_1S_0	X_2X_1			
	00	01	11	10
00	0	0	X	0
01	0	0	X	X
11	0	0	X	1
10	1	0	X	0

$S_2 = 0$

S_1S_0	X_2X_1			
	00	01	11	10
00	1	X	X	1
01	1	0	X	1
11	1	1	X	1
10	1	1	X	1

$S_2 = 1$

$$S'_2 = \overline{S_2}(S_1\overline{S_0}X_2X_1 + S_0X_2) + S_2(S_1 + \overline{X_1} + \overline{S_0})$$

K-map for S'_1 :

		X_2X_1			
		00	01	11	10
S_1S_0	00	0	0	X	1
	01	1	0	X	X
	11	1	1	X	1
	10	1	1	X	1

$S_2 = 0$

		X_2X_1			
		00	01	11	10
S_1S_0	00	1	X	X	0
	01	0	0	X	0
	11	0	1	X	1
	10	1	1	X	1

$S_2 = 1$

$$S'_1 = \overline{S_2}(\overline{S_0}\overline{X_1} + S_1 + X_2) + S_2(\overline{S_0}X_2 + S_1X_1 + S_1X_2)$$

K-map for S'_0 :

		X_2X_1			
		00	01	11	10
S_1S_0	00	0	1	X	0
	01	1	1	X	X
	11	1	0	X	1
	10	0	0	X	0

$S_2 = 0$

		X_2X_1			
		00	01	11	10
S_1S_0	00	0	X	X	0
	01	1	1	X	0
	11	1	1	X	1
	10	0	1	X	1

$S_2 = 1$

$$S'_0 = \overline{S_2}(\overline{S_0}\overline{X_1} + \overline{S_1}X_1 + \overline{S_1}S_0) + S_2(\overline{S_0}\overline{X_2} + X_1 + S_1X_2)$$

Notice that we have added extra grouping that overlaps with other groups (highlighted in cyan color). These additional groups are necessary to remove hazards in circuit. Here is a circuit if these groupings are not done: [Click here](#). Notice that circuit oscillates by default. It will also oscillate if you switch X_1 .

7 Output expression

Since output $z = 1$ only when current state is G , so a separate "output transition table" is not drawn. We can directly write (from binary assignment for G) that:

$$z = S_2\overline{S_1}S_0$$

8 Circuit

[Click here to see simulation in Falstad](#)

